

Class 12 - Important Formulas

Chapter 7 - Alternating Current

S.No.	Term	Description
1	Alternating current	It is current whose magnitude changes with time and direction reverses periodically. $I = I_0 \sin \omega t$ where I_0 is the peak value of a.c. and $\omega = 2\pi/T$ is the frequency
2	Mean value of a.c.	$I_m = 2I_0/\pi = 0.636I_0$
3	RMS value	$I_{rms} = I_0/\sqrt{2}$
4	a.c. through resistor	Alternating emf is in phase with current
5	a.c. through inductor	Emf leads the current by an phase angle $\pi/2$
6	a.c. through capacitor	Emf lags behind the current by an phase angle $\pi/2$
7	Inductive reactance	Opposition offered by inductor to the flow of current mathematically, $X_L = \omega L = 2\pi fL$
8	Capacitive reactance	Opposition offered by capacitor to the flow of current mathematically, $X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$
9	a.c. through series LR circuit	Emf leads the current by an phase angle ϕ given by $\tan \phi = \frac{\omega L}{R}$ and impedance of circuit is $Z = \sqrt{R^2 + (\omega^2 L^2)}$
10	a.c. through series CR circuit	Emf lags behind the current by an phase angle ϕ given by $\tan \phi = \frac{1/\omega C}{R}$ and impedance of circuit is $Z = \sqrt{R^2 + \left(\frac{1}{\omega^2 C^2}\right)}$
11	a.c. through series LCR circuit	Emf leads/lags behind the current by an phase angle ϕ given by $\tan \phi = \frac{\omega L - 1/\omega C}{R}$ emf leads the current when $\omega L > \frac{1}{\omega C}$ and lags behind when $\omega L < \frac{1}{\omega C}$ and impedance of circuit is $Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$
12	Average power of an a.c. circuit	$P_{avg} = I_{rms}^2 R = E_{rms} I_{rms} \cos \phi$ Where ϕ is called power factor of the circuit.
13	Transformer	It is a device used to change low alternating voltage at high current into high voltage at low current and vice-versa. Primary and secondary voltage for a transformer are related as $V_s = V_p \frac{N_s}{N_p}$ and current through the coils is related as $I_s = I_p \frac{N_p}{N_s}$